

Total Pages : 4

Roll No. ....

# **PHY-504**

## **Semiconductor Devices, Analog and Digital Electronics**

M.Sc. PHYSICS (MSCPHY-12/13/16/17)

First Year, Examination, 2019 (June)

**Time : 3 Hours]**

**Max. Marks : 80**

**Note :** This paper is of Eighty (80) marks divided into three (03) sections A, B and C. Attempt the questions contained in these sections according to the detailed instructions given therein.

### **SECTION-A**

**(Long Answer Type Questions)**

**Note :** Section 'A' contains four (04) long answer type questions of Nineteen (19) marks each. Learners are required to answer any two (02) questions only.

$$(2 \times 19 = 38)$$

1. Describe the working of P-N junction diode under forward and reverse biasing.
2. Give the theory of operational Amplifier and its characteristics parameters.
3. Give the theory and applications of De-Morgan's theorems.

- 4.** Give classification of oscillators in brief and derive Barkhausen condition to maintain oscillations in feedback oscillator.

## **SECTION-B**

### **(Short Answer Type Questions)**

**Note :** Section 'B' contains eight (08) short answer type questions of eight (08) marks each. Learners are required to answer any four (04) questions only.      ( $4 \times 8 = 32$ )

- 1.** Give the expression for width of depletion layer in junction diode.
- 2.** Explain the biasing of P-N junction diode.
- 3.** Explain amplifiers and their classification.
- 4.** Why a part of output is fed back as signal in amplifiers ?
- 5.** Explain why a power amplifier is called a large signal amplifier ?
- 6.** Explain the distortions produced in class A and push-pull amplifiers.
- 7.** Write a short note on octal system.
- 8.** Give the truth table for binary multiplication.

## SECTION-C

### (Objective Type Questions)

**Note :** Section 'C' contains ten (10) objective type questions of one (01) mark each. All the questions of this section are compulsory.  $(10 \times 1 = 10)$

- 1.** P-type semiconductor material is :
  - (a) silicon doped with indium
  - (b) silicon
  - (c) silicon doped with arsenic
  - (d) germanium.
  
- 2.** When a diode is heavily doped
  - (a) the Zener voltage will be low
  - (b) the Avalanche voltage will be high
  - (c) the depletion region will be thin
  - (d) the leakage current will be low.
  
- 3.** A regulated power supply consists of
  - (a) A power transformer
  - (b) A full wave rectifier
  - (c) A smoothing filter
  - (d) A voltage regulator circuit.
  
- 4.** In a transistor with normal bias, the emitter junction
  - (a) is reversed biased
  - (b) has a high resistance
  - (c) has a low resistance
  - (d) is forward biased.

- 5.** The voltage gain of a common base amplifier depends upon
- (a) load resistor  $R_L$
  - (b) input resistance of transistor
  - (c) a.c. alpha
  - (d) All the above.
- 6.** Maximum theoretical conversion efficiency of a class-B push-pull amplifier is :
- (a) 25%
  - (b) 50%
  - (c) 78.5%
  - (d) 85.6%.
- 7.** Introduction of negative feedback in an amplifier increases
- (a) gain
  - (b) noise level
  - (c) band-width
  - (d) harmonic distortion.
- 8.** In an a stable multivibrator
- (a)  $\beta = 1$
  - (b)  $\beta > 1$
  - (c)  $\beta < 1$
  - (d)  $\beta A = 1$ .
- 9.** A FET has a :
- (a) source
  - (b) gate
  - (c) drain
  - (d) all of the above.
- 10.** The output of UJT can be taken from its :
- (a) base 1
  - (b) base 2
  - (c) emitter
  - (d) any one of three terminals.
-