

BLOCK – II OPERATIONAL AMPLIFIERS

UNIT 8: Operational Amplifier and its characteristics parameters



Dr. Meenakshi Rana

Academic Consultant

Department of Physics

Uttarakhand Open University, Haldwani


Content

- 1. Introduction.**
- 2. What is op-amp.**
- 3. Circuit symbol.**
- 4. Operational Amplifiers picture.**
- 5. Pin Diagram.**
- 6. Application of op-amp.**
- 7. Ideal op-amp.**
- 8. Non ideal op-amp.**
- 9. Characteristics of op-amp.**
- 10. Important terms and equation.**


Introduction

The term “**operational amplifier**” denotes a special type of amplifier that, by proper selection of its external components, could be configured for a variety of operations.

Schematic Symbol

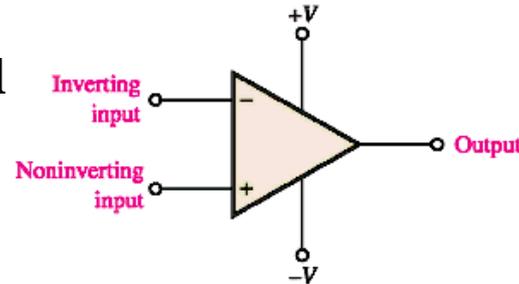

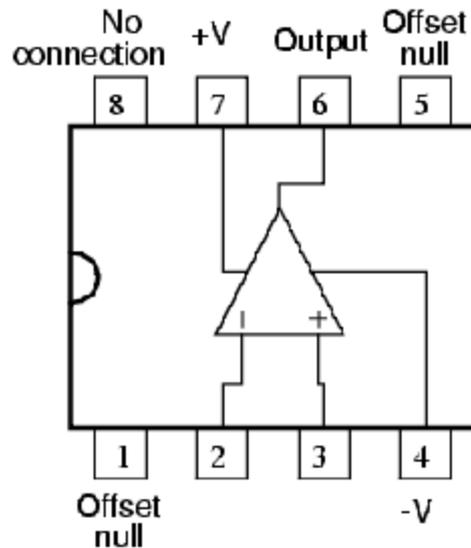The two input terminals, called the inverting and non-inverting, are labeled with – and +, respectively



Two Power Supply (PS)

- +V : Positive PS
- V : Negative PS

One Output Terminal


Two Input Terminals

- Inverting input
- Non-inverting input

Op amps are differential amplifiers, and their output voltage is proportional to the difference of the two input voltages.

History

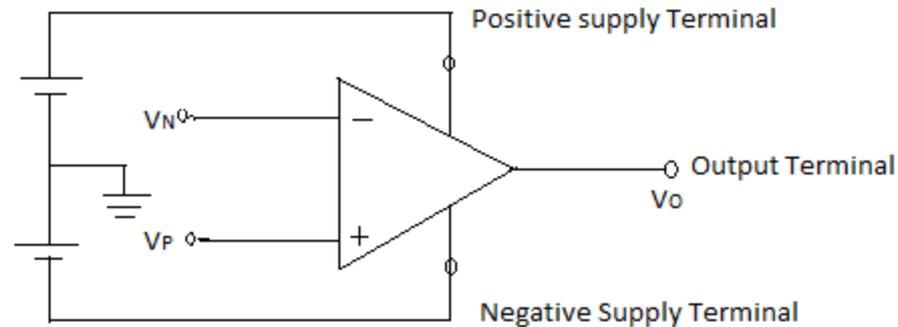- First developed by **John R. Ragazzine** in 1947 with vacuum tube.
- In 1960 at **FAIRCHILD SEMICONDUCTOR CORPORATION**, **Robert J. Widlar** fabricated op amp with the help of IC fabrication technology.
- In 1968 FAIRCHILD introduces the **op-amp** that was to become the industry standard.



Ckt symbol for general purpose op-amp

Figure shows the symbol of op-amp & the power supply connections to make it work. The input terminal identified by the '-' and "+" symbols are designated inverting & noninverting.

Their voltage w.r.t ground are denoted as V_N & V_P and output voltage as V_O . **Op-amp** do not have a zero volt ground terminal Ground reference is established externally by the power supply common.

Operational Amplifiers picture



Figure: The Philbrick Operational Amplifier.



Figure : What an Op-Amp looks like in today's world

Op-amp pin diagram

- Pin 1: Offset null
- Pin 2: Inverting input terminal
- Pin 3: Non-inverting input terminal
- Pin 4: $-V_{CC}$ (negative voltage supply)
- Pin 5: Offset null
- Pin 6: Output voltage
- Pin 7: $+V_{CC}$ (positive voltage supply)
- Pin 8: No Connection

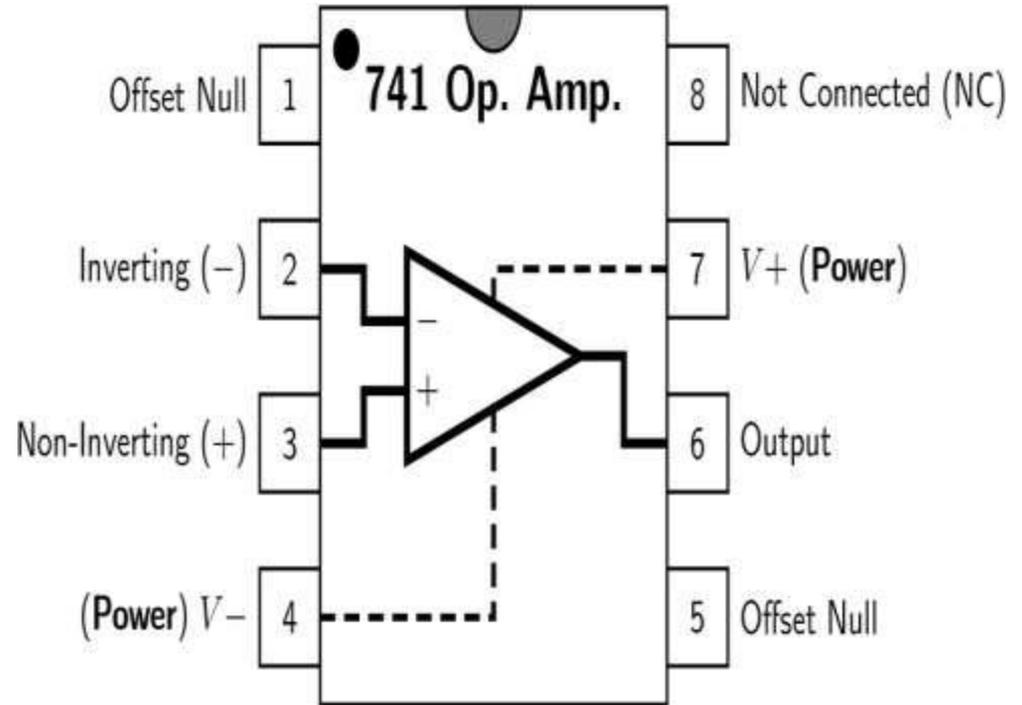


Figure : Pin connection, LM741.

Applications of Op-Amp

- To provide voltage amplitude changes (amplitude and polarity)
- Comparators
- Oscillators
- Filters
- Sensors
- Instrumentation amplifiers

Characteristics of an Ideal Operational

Characteristics of an Ideal Operational amplifier Ideal

op-amp has following characteristics -

Input Resistance $R_i = \infty$

Output Resistance $R_o = 0$

Voltage Gain $A = \infty$

Bandwidth = ∞

Perfect balance i.e $v_o = 0$ when $v_1 = v_2$

Characteristics do not drift with temperature

Properties

Ideal Op-Amp

Infinite input impedance

Zero output impedance

Infinite open-loop gain

Infinite bandwidth

Zero noise contribution

Zero DC output offset

Practical Op-Amp

Input impedance 500k-2MW

Output impedance 20-100 W

Open-loop gain (20k to 200k)

Bandwidth limited (a few kHz)

Has noise contribution

Non-zero DC output offset

Zero Noise Contribution

- In an ideal op amp, all noise voltages produced are external to the op amp.

Thus any noise in the output signal must have been in the input signal as well.

- The ideal op amp contributes nothing extra to the output noise.

- In real op-amp, there is noise due to the internal circuitry of the op-amp that contributes to the output noise.

Op-Amp Parameters

COMMON-MODE REJECTION (CMRR)

COMMON-MODE INPUT VOLTAGE

INPUT OFFSET VOLTAGE

INPUT BIAS CURRENT

INPUT IMPEDANCE

INPUT OFFSET CURRENT

OUTPUT IMPEDANCE

SLEW RATE

Common-Mode Rejection Ratio (CMRR)

□ The ability of amplifier to reject the common-mode signals (unwanted signals) while amplifying the differential signal (desired signal).

□ Ratio of open-loop gain, A_{ol} to common-mode gain, A_{cm}

$$CMRR = A_{ol}/A_{cm}$$

$$CMRR = 20 \log(A_{ol}/A_{cm})$$

□ The higher the CMRR, the better, in which the open-loop gain is high and common-mode gain is low.


□ CMRR is usually expressed in dB & decreases with frequency.

Input Offset Voltage

- ❑ Ideally, output of an op-amp is 0 Volt if the input is 0 Volt.
- ❑ Realistically, a small dc voltage will appear at the output when no input voltage is applied.
- ❑ Thus, differential dc voltage is required between the inputs to force the output to zero volts.
- ❑ This is called the Input Offset Voltage, V_{os} . Range between 2 mV or less.


Input Bias Current

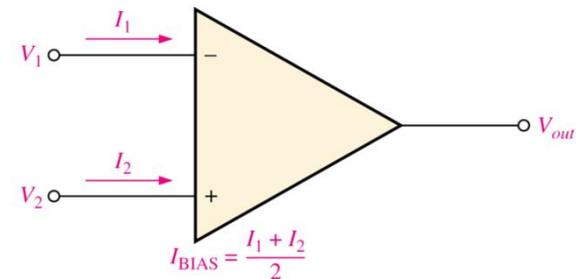- ❑ Ideally should be zero.
- ❑ The dc current required by the inputs of the amplifier to properly operate the first stage.
- ❑ Is the average of both input currents.




Input Impedance

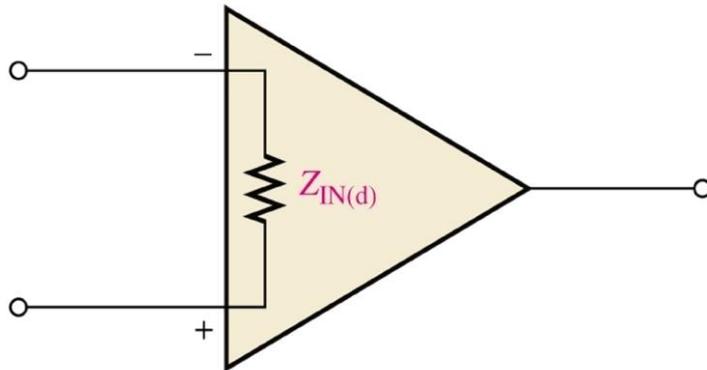- Is the total resistance between the inverting and non-inverting inputs.
- Differential input impedance : total resistance between the inverting and non-inverting inputs.
- Common-mode input impedance: total resistance between each input and ground.




(a) Differential input impedance

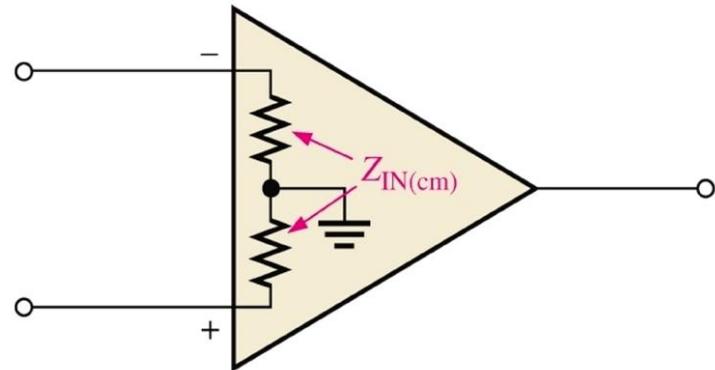

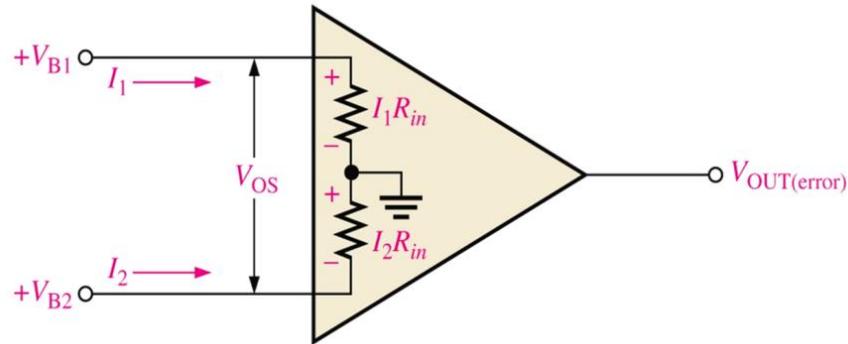(b) Common-mode input impedance

Input Offset Current

It is the difference of input bias currents.



Input offset current

$$I_{os} = |I_1 - I_2|$$

Thus, error

$$V_{out(error)} = A_v I_{os} R_{in}$$


Offset voltage

$$V_{os} = I_1 R_{in} - I_2 R_{in} = (I_1 - I_2) R_{in}$$

$$V_{os} = I_{os} R_{in}$$


Slew Rate

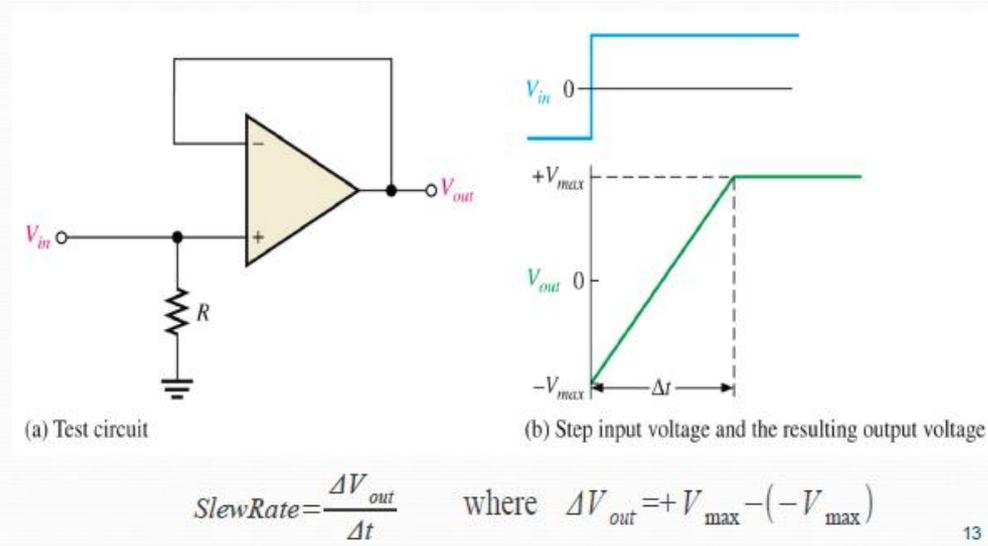□ It is the maximum rate of change of the output voltage in response to a step input voltage.




Slew Rate

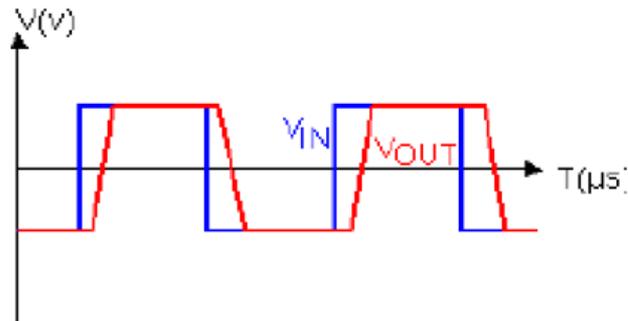□ It's a measure of how fast the output can “follow” the input signal.



Example

Determine the slew rate:

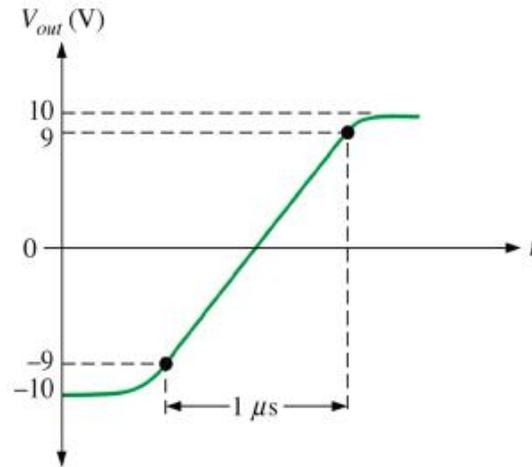

$$SlewRate = \frac{\Delta V_{out}}{\Delta t}$$

$$SlewRate = \frac{+9V - (-9V)}{1\mu s} = 18V/\mu s$$

Some Useful links

<https://nptel.ac.in/content/storage2/courses/108101091/Week%206%20Slides.pdf>

<https://www.youtube.com/watch?v=kiiA6WTCQno>

<https://www.youtube.com/watch?v=AuZoocQoUrE>

youtube.com/watch?v=kiiA6WTCQno&list=PLwjK_ iyK4LLDBB1E9MFbxGCEnmMMOAXOH

Thanks