# **PHY-504**

## Semiconductors Devices, Analog and Digital Electronics

M. Sc. PHYSICS (MSCPHY–12/13/16) First Year, Examination, 2017

#### Time : 3 Hours

#### Max. Marks: 80

Note: This paper is of eighty (80) marks containing three (03) Sections A, B and C. Learners are required to attempt the questions contained in these Sections according to the detailed instructions given therein.

## Section-A

## (Long Answer Type Questions)

- **Note :** Section 'A' contains four (04) long answer type questions of nineteen (19) marks each. Learners are required to answer *two* (02) questions only.
- 1. What do you mean by N-type and *p*-type semiconductor. Explain with the help of diagram how free electrons and holes contribute to electric current.
- 2. Define  $\alpha$  and  $\beta$  of a transistor and derive relationship between them. Sketch a family of common emitter output characteristics for a transistor. Clearly indicate the cut off, active and saturation regions.
- 3. State and prove De-Morgan's theorem. Discuss the working of half adder and full adder and give their truth table.

#### Section-B

## (Short Answer Type Questions)

- **Note :** Section 'B' contains eight (08) short answer type questions of eight (08) marks each. Learners are required to answer *four* (04) questions only.
- 1. Draw the block diagram of a regulated power supply and explain each block in detail.
- 2. Show that both NAND gate and NOR gate are universal gates.
- 3. Realize X-OR operation using :
  - (a) Only NAND gates
  - (b) Only NOR gates
- 4. What is Op-amp. ? Draw equivalent circuit of an Opamp. (Operational amplifier). Write ideal characteristic of Op-amp.
- 5. Draw the circuit diagram of Op-amp. as Summer and find out the expression for output.
- With the help of neat diagram explain the working of R-2R ladder network type digital to analog converter (DAC).
- Compare Asynchronous and Synchronous Counter. Design a Mod-10 asynchronous counter using T Flip-Flop.
- 8. With the help of logic diagram and function table explain a 4-input multiplexer.

#### [3]

## Section-C

## (Objective Type Questions)

- **Note :** Section 'C' contains ten (10) objective type questions of one (01) mark each. All the questions of this Section are compulsory.
- 1. ASCII code is a :
  - (a) 5-bit code
  - (b) 7-bit code
  - (c) 8-bit code
  - (d) 10-bit code
- 2. The fastest ADC (Analog to Digital Converter) is :
  - (a) Counter-type
  - (b) Flash type
  - (c) Successive approximation type
  - (d) Dual slope type
- 3. How many states a 6-bit ripple counter can have ?
  - (a) 6
  - (b) 12
  - (c) 32
  - (d) 64
- 4. The negative feedback in amplifier :
  - (a) reduces the voltage gain
  - (b) increases the voltage gain
  - (c) does not affect the voltage gain
  - (d) None of the above

- 5. A load line is a graph between :
  - (a)  $I_C$  and  $V_{CC}$
  - (b)  $I_C$  and  $V_{CE}$
  - (c)  $I_E$  and  $V_{BE}$
  - (d)  $I_C$  and  $V_{BE}$
- 6. Wien bridge oscillator uses :
  - (a) Positive feedback
  - (b) Negative feedback
  - (c) Both positive and negative feedback
  - (d) No feedback
- 7. The voltage gain of transistor amplifier is lowest in :
  - (a) CE configuration
  - (b) CB configuration
  - (c) CC configuration
  - (d) None of the above
- 8. The voltage gain of ideal voltage follower is :
  - (a) 1 (b) <1
  - (c) 0 (d) Infinity
- 9. The ideal value of Common Mode Rejection Ratio (CMRR) is :
  - (a) 1 (b) 0
  - (c)  $\infty$  (d)  $-\infty$
- 10. The no. of flip-flops required in a decade counter is :
  - (a) 2 (b) 3
  - (c) 4 (d) 10

PHY-504