

Total Pages : 03

Roll No. : .....

**MCA-02/PGDCA-02/M.Sc.IT-02**

**Digital Logic**

**Master/P.G.Diploma in Computer Application/  
Master of Science in Information Technology/Master of  
Science (Cyber Security)**

1<sup>st</sup> /3<sup>rd</sup> Semester Examination June 2022

Time : 2 Hours

Max. Marks : 80

Note : This Paper is of Eighty (80) marks divided into two (02) Section A and B. Attempt the questions contained in these sections according to the detailed instructions given there in.

Section-A

(Long Answer-type questions)

Note: Section 'A' contains Five (05) Long-answer type questions of Twenty (20) marks each. Learners are required to answer any two (02) questions only.

(2 x 20 = 40)

P.T.O.

- Q.1. Discuss and design 2 bit up/down synchronous counter with suitable diagram ?
- Q.2 What is full adder? Draw a full adder using two half adder and gives its truth table.
- Q.3 What do you understand by K map? Explain its application using suitable example.
- Q.4 What do you understand by SR-flip flop and T flip flop? Explain the difference between Jk-flip flop and D flip flop with their characteristic table.
- Q.5 Explain the following keywords:  
a. Gray code                      b. Encoder                      c. Decoder

### Section-B

(Short Answer-type questions)

Note: Section 'B' contains Eight (08) Short-answer type questions of ten (10) marks each. Learners are required to answer any four (04) questions.

(4 x 10 = 40)

- Q.1 What is difference between RAM and ROM?

P.T.O.

- Q.2 Simplify  $F(x,y,z)=\sum m(2,3,4,6,7)$  using K-map.
- Q.3 Convert the following numbers from the given base to the base indicated:
- $(A56)_{16}=(?)_{10}$
  - $(101101)_2=(?)_8$
- Q.4 What do you understand by don't care condition ?
- Q.5 Write about the different types of logical gates.
- Q.6 What are the Boolean laws?
- Q.7 If P,Q, R are Boolean variables, then simplifies the following expression :
- $$(P + Q')(PQ' + PR)(P'R' + Q')$$
- Q.8 What do you understand by De-Morgan's Theorem?  
Explain with example.

.....