Roll No.

# **PHY-504**

## Semiconductor Devices, Analog and Digital Electronics

M. Sc. PHYSICS (MSCPHY-12/13/16)

First Year, Examination, 2017

#### Time : 3 Hours

#### Max. Marks: 70

Note: This paper is of seventy (70) marks containing three (03) sections A, B and C. Attempt the questions contained in these sections according to the detailed instructions given therein.

#### Section-A

### (Long Answer Type Questions)

- **Note :** Section 'A' contains four (04) long answer type questions of fifteen (15) marks each. Learners are required to answer *two* (02) questions only.
- 1. Explain with the help of neat diagrams, the structure of a N-channel FET and its volt ampere characteristics. In what ways it is different from a bipolar junction transistor ?
- 2. Setup an analog computer in block diagram using opamp to solve the following differential equations :

(i) 
$$\frac{d^2y}{dt^2} + 6\frac{dy}{dt} + 6.8y + c(t) = 0$$

(ii)  $\frac{d^2 V}{dt^2} + 6\frac{dV}{dt} + 3V - V_i = 0$ 

(iii) 
$$\frac{d^2y}{dt^2} + 3\frac{dy}{dt} + 2y = 3\sin t$$

where  $V_i$  is a given function of time.

2. Calculate the (i) operating frequency and (ii) feedback fraction for Hartley oscillator shown in Fig. The mutual inductance between the coils,  $M = 20\mu$ H.



4. Explain R-2R ladder networks in details with circuit diagrams.

#### Section-B

#### (Short Answer Type Questions)

- **Note :** Section 'B' contains eight (08) short answer type questions of five (5) marks each. Learners are required to answer *six* (06) questions only.
- 1. Draw the circuit diagram of bridge rectifier and explain in brief.

- 2. Explain the concept of feedback with the help of neat circuit diagrams.
  - 3. With the help of circuit diagram, explain the working of a 4-bit subtractor.
  - 4. Simplify the Boolean function with map :

 $f(x, y, z) = \Sigma(3, 4, 6, 7)$ 

- 5. State and prove De-Morgan's laws.
- 6. Explain digital to analog converters with example.
- 7. Explain the difference between synchronous and asynchronous counter.
- 8. What is a varactor diode ? Explain its action.

## Section-C

## (Objective Type Questions)

**Note :** Section 'C' contains ten (10) objective type questions of one (01) mark each. All the questions of this section are compulsory.

Choose the correct alternative.

- 1. A device uses small amount of energy to control large amount of energy is :
  - (a) Transistor
  - (b) Diode
  - (c) Resistor
  - (d) Amplifier
- 2. Transistor consists of :
  - (a) Emitter, Base, Collector
  - (b) Electron, Proton, Neutron
  - (c) Resistor, Capacitor coil
  - (d) None of the above

- (a) 10.24 kHz
- (b) 5 kHz
- (c) 30.24 kHz
- (d) 15 kHz
- 4. Which of the following logical operations is represented by + sign in Boolean Algebra ?
  - (a) Inversion
  - (b) AND
  - (c) OR
  - (d) Complementation
- 5. How many flip-flops are required to construct a decade counter ?
  - (a) 10
  - (b) 8
  - (c) 5
  - (d) 4
- 6. To implement the expression  $\overrightarrow{ABCD} + \overrightarrow{ABCD}$ + $\overrightarrow{ABCD}$ , it takes one OR gate and .....
  - (a) Three AND gates and three NOT gates
  - (b) Three AND gates and four NOT gates
  - (c) Three AND gates
  - (d) One AND gate

[5]

Fill in the blanks.

- 7. MOSFET means .....
- 8. CMOS means .....
- 9. ..... is an electronic device that converts energy from one form to another.
- 10. ..... is a measure for the degree a component resist the flow of the electrical current in given voltage.

#### **PHY-504**